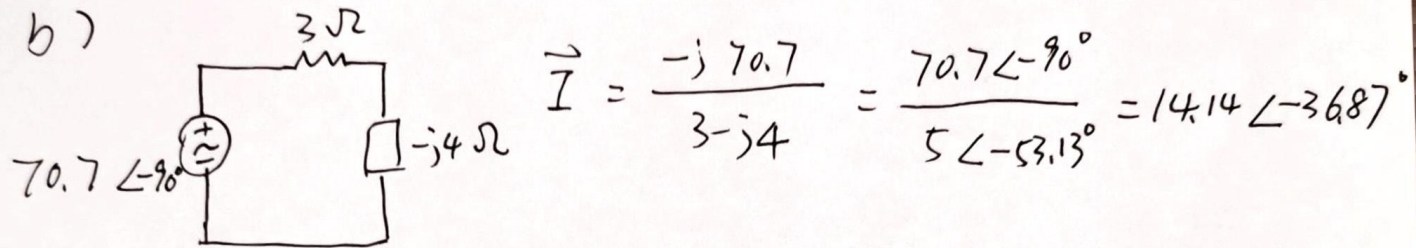


1. a)  $Z_T = 3 + j\omega L + \frac{1}{j\omega C} = 3 + j \times 10^4 \times 600 \times 10^{-6} + \frac{1}{j \times 10^4 \times 10 \times 10^{-6}}$

$$= 3 - j4 \Omega$$



$$i(t) = 14.14 \cos(10^4 t - 36.87^\circ) \text{ A}$$

c)  $\vec{V}_L = \vec{I} \cdot Z_L = 14.14 e^{-j36.87^\circ} \times 6 e^{j90^\circ} = 84.84 e^{j53.13^\circ} \text{ V}$

$$\vec{V}_R = \vec{I} \cdot R = 42.42 \angle -36.87^\circ \text{ V}$$

$$\vec{V}_C = \vec{I} \cdot Z_C = 14.14 e^{-j36.87^\circ} \cdot (10 e^{j90^\circ}) = 141.4 e^{-j126.87^\circ} \text{ V}$$

$$V_R(t) = 42.42 \cos(10^4 t - 36.87^\circ) \text{ V}$$

$$V_L(t) = 84.84 \cos(10^4 t + 53.13^\circ) \text{ V}$$

$$V_C(t) = 141.4 \cos(10^4 t - 126.87^\circ) \text{ V}$$

d) If frequency doubles.  $Z_T = 3 + j \cdot 12 - j5 = 3 + j7 \Omega$


the magnitude increases  
of  $Z_T$

current peak value decreases.

phase angle is  $\tan^{-1}(\frac{7}{3}) = 66.88^\circ$ , current lags voltage.

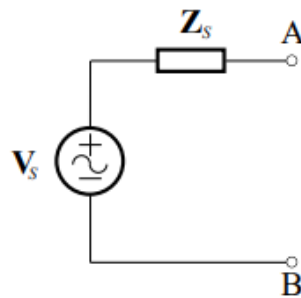2.

Simplify the circuit by applying Thévenin's Theorem to terminals A and B:




The Thévenin voltage  $V_s$  is the open-circuit voltage. Using the voltage divider rule we get:

$$V_s = \frac{2 + j5}{2.4 + j5.8} \times 100 \angle 0^\circ = \frac{5.385 \angle 68.20^\circ}{6.277 \angle 67.52^\circ} \times 100 \angle 0^\circ = 85.79 \angle 0.678^\circ \text{ V}$$

Setting the independent voltage source to zero, looking into terminals A and B we see two impedances in parallel:

$$\begin{aligned} Z_s &= (0.4 + j0.8) \parallel (2 + j5) = \frac{-3.2 + j3.6}{2.4 + j5.8} = \frac{4.817 \angle 131.6^\circ}{6.277 \angle 67.52^\circ} \\ &= 0.7673 \angle 64.08^\circ \Omega = 0.3350 + j0.6904 \Omega \end{aligned}$$

The equivalent circuit is now:

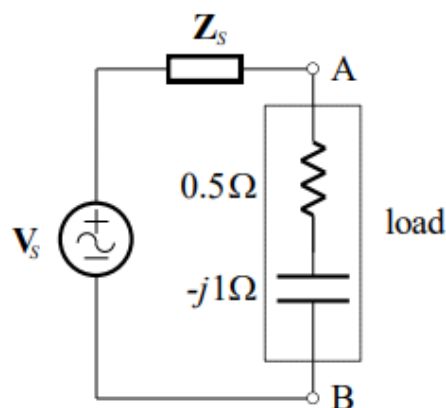

The load current is then given by Ohm's Law:

$$I_L = \frac{V_s}{Z_s + Z_L} = \frac{85.79 \angle 0.678^\circ}{0.3350 + j0.6904 + 0.5 - j} = \frac{85.79 \angle 0.678^\circ}{0.8905 \angle -20.34^\circ} = 96.33 \angle 21.02^\circ \text{ A}$$

The voltage between terminals A and B is given by Ohm's Law:

$$\begin{aligned} V_L &= Z_L I_L = (0.5 - j) \times 96.33 \angle 21.02^\circ = 1.118 \angle -63.43^\circ \times 96.33 \angle 21.02^\circ \\ &= 107.7 \angle -42.41^\circ \text{ V} = 79.52 - j72.64 \text{ V} \end{aligned}$$