

1.

$$V = L \times \frac{di}{dt} = 2 \times \frac{d(5 \sin 10t)}{dt} = 100 \cos 10t$$


$$P = V \times i = 5 \sin 10t \times 100 \cos 10t = 250 \sin 20t \Rightarrow T = \frac{2\pi}{20} = 314.2 \text{ ms}$$

(a)  $250 \sin 20t = 100 \Rightarrow t = 20.6 \text{ ms}$

(b)  $250 \sin 20t = -100 \Rightarrow t = 177.7 \text{ ms}$



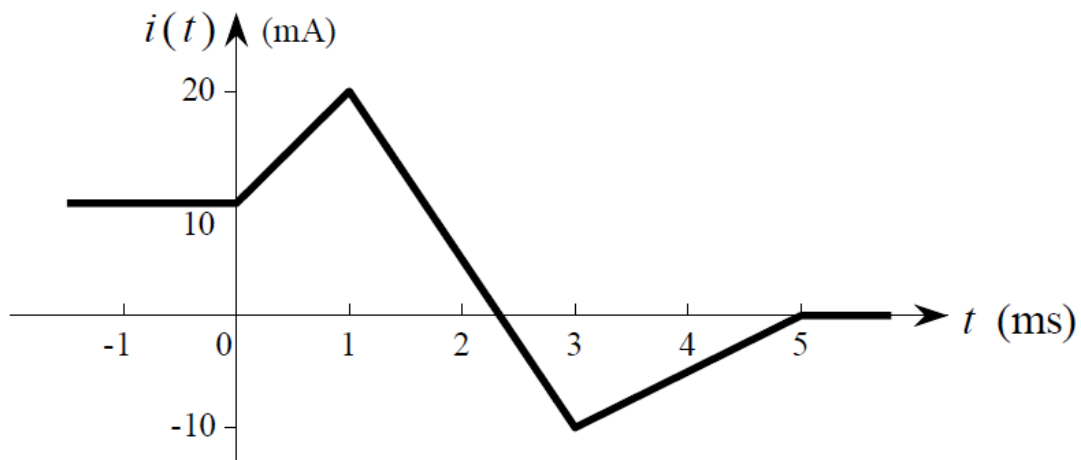2. The variation of current through a 25 mH inductor as a function of time is shown below, please find the voltage across the inductor.



Solution:

Since the current is constant for  $t < 0$ , the voltage is zero in this interval. The current then begins to increase at the linear rate  $di/dt = 10 \text{ As}^{-1}$ , and thus a constant voltage of  $v = L di/dt = 250 \text{ mV}$  is produced. During the following 2 millisecond interval, the current decreases at the linear rate  $di/dt = -15 \text{ As}^{-1}$ , and so the voltage is  $v = L di/dt = -375 \text{ mV}$ . The final increase of the current causes a positive 125 mV and no response thereafter. The voltage waveform is sketched below:

